

Excitation Control System & Dynamic Brake)


S.K.Sinha/CI(DSL)

OBJECTIVE: Excitation System

- ▶ What is Electrical Transmission
- ▶ Voltage & Current limit
- ▶ constant power transmission
- ▶ Excitation Control System
- ▶ Main Components: Exciter Gen, Control Panel, Magnetic Amplifier
- ▶ Basic E -Type Excitation control System


ELECTRICAL POWER TRANSMISSION -BASIC REQUIREMENTS

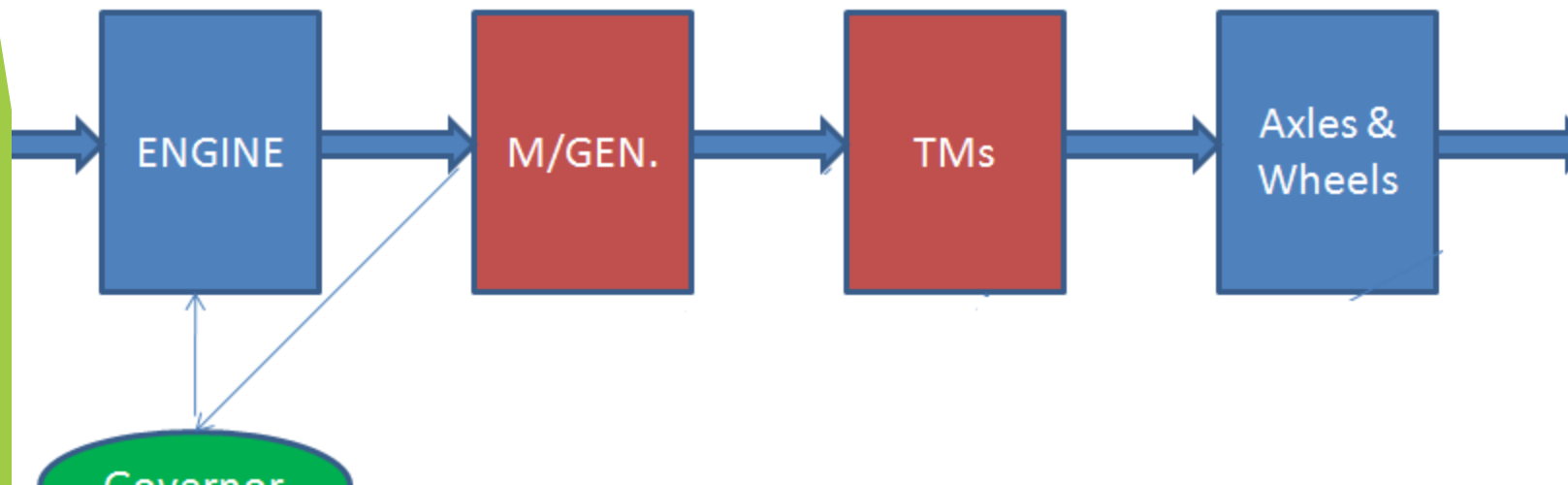- ▶ Voltage & Current be under limitations.
- ▶ Power transmission be constant



BASIC REQUIREMENTS- VOLTAGE & CURRENT LIMITS

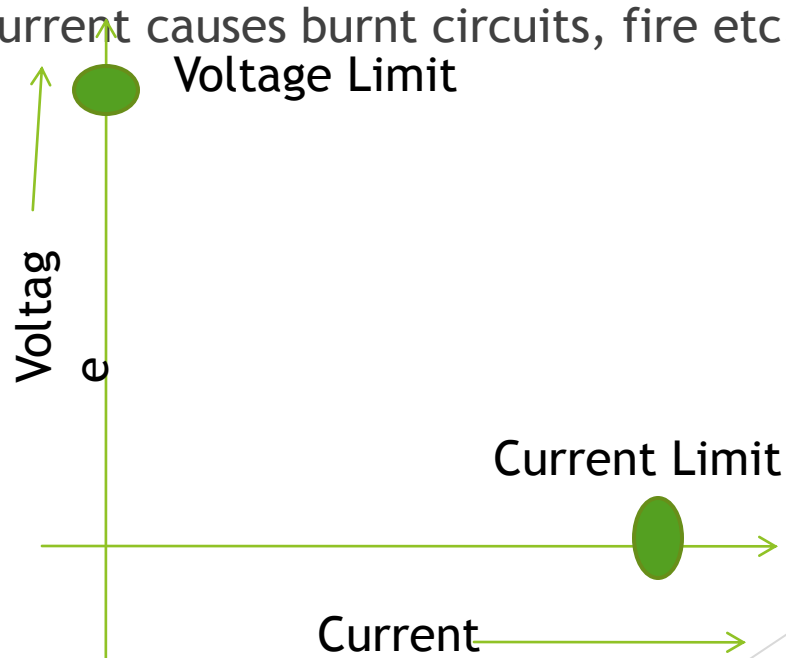- ▶ Very high voltage causes insulation break down., Flash over etc.
- ▶ Very large Current causes burnt circuits, fire etc.




BASIC REQUIREMENTS- CONSTANT POWER TRANSMISSION

- ▶ **Means**

$$P=V I=\text{constant}$$

- ▶ **Causes**


better Sp. Fuel efficie

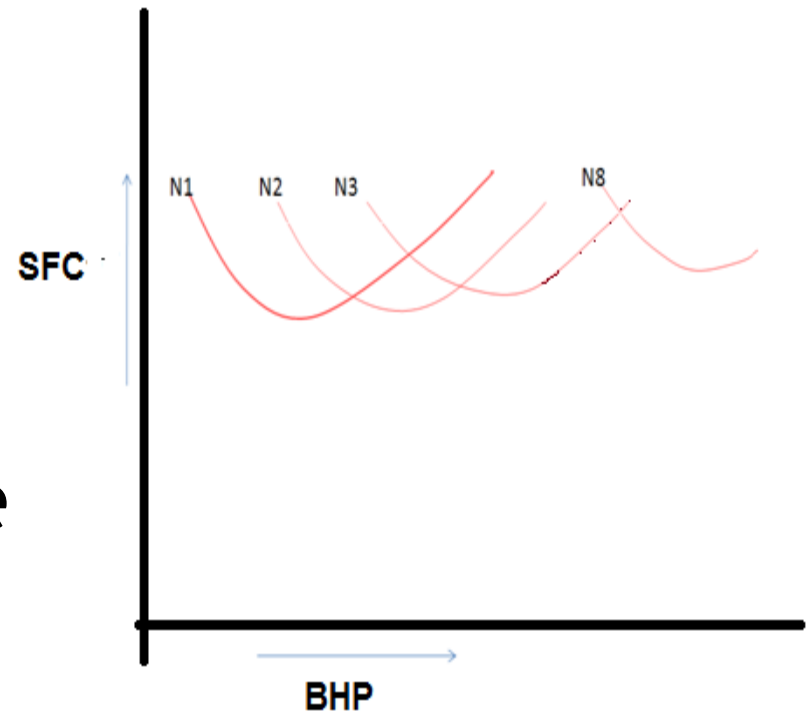

JOB OF AN EXCITATION CONTROL SYSTEM



Maintains-

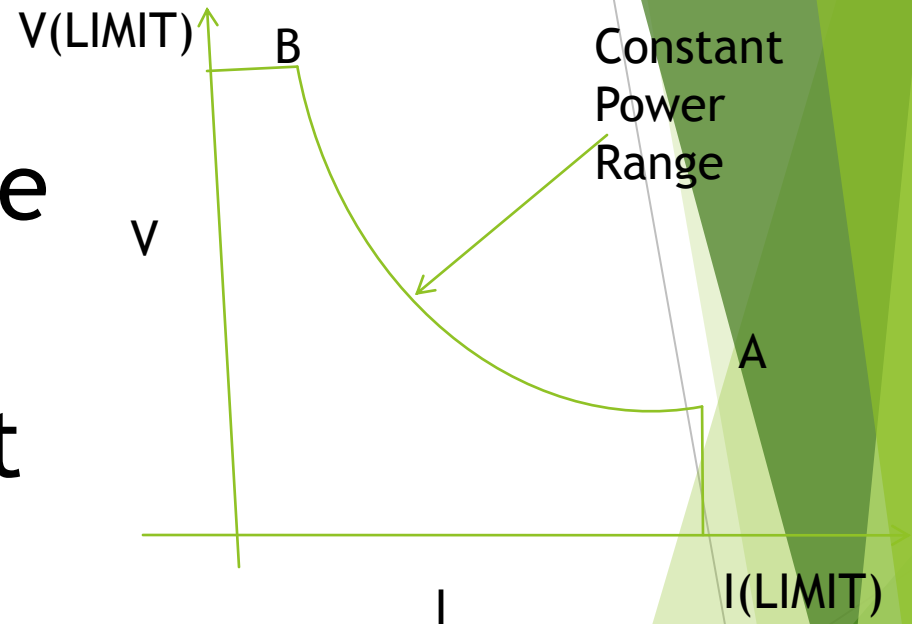- maximum voltage limit
- maximum current limit
- constant power transmission




A TYPICAL GENERATOR LOAD CURVE (FOR 8th NOTCH)-WITH EXCITATION SYSTEM

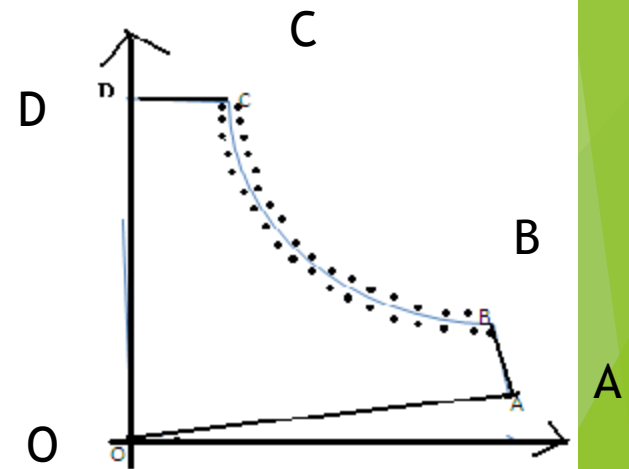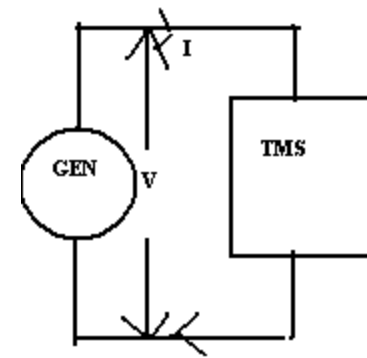- ▶ OA → IR line
(when the train is not moving)
- ▶ AB → the current limit of the Gen.
- ▶ BC → constant rated engine HP
- ▶ Dotted lines -System tolerance (2.1/2%)
- ▶ CD → Voltage limit



FAMILY OF NOTCH CURVES

1st Notch through 8th Notch

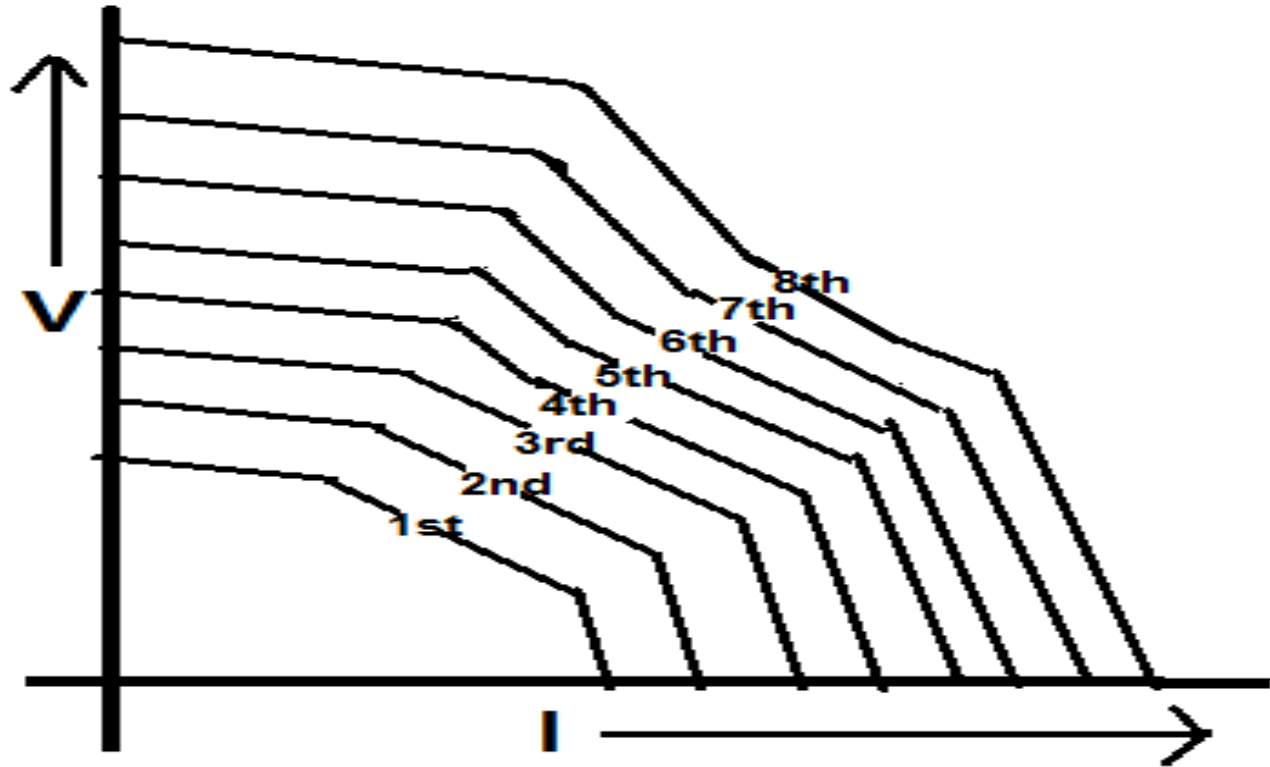


Electronics Excitation System-Main Components

- ▶ Exciter Generator
- ▶ Excitation Control Panel
- ▶ Magnetic Amplifiers

EXCITER GENERATOR

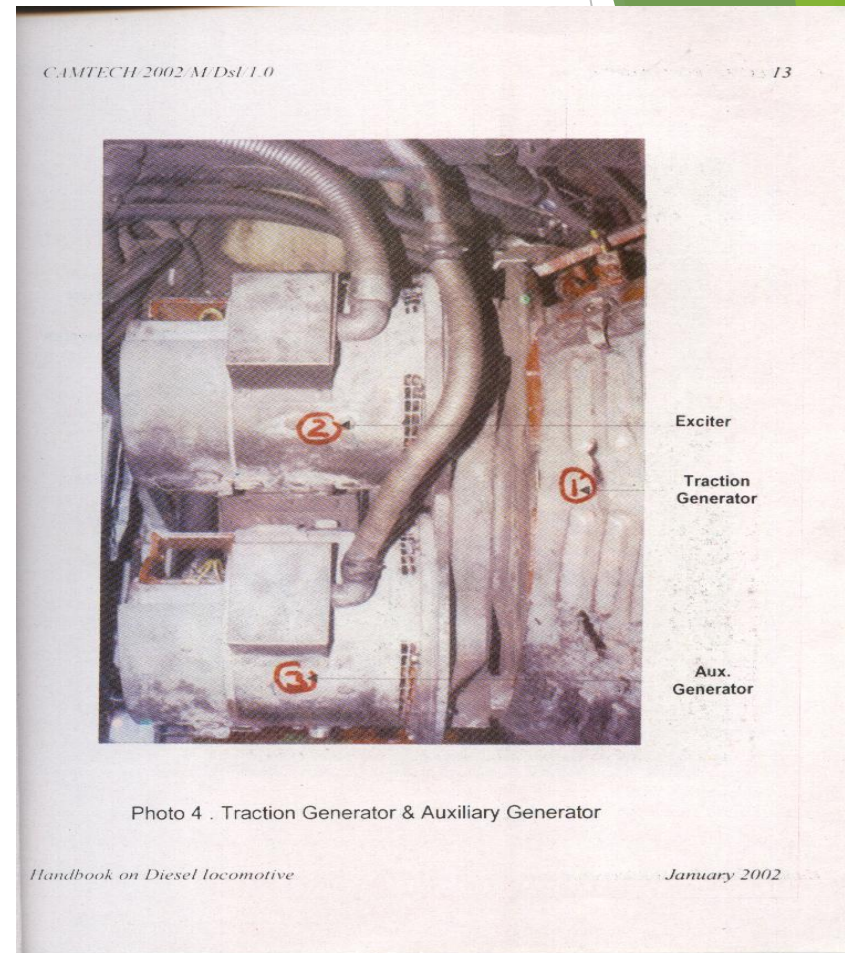- ▶ A 4-Pole separately excited d-c Generator
- ▶ Mounted on the Tr.Gen/Alt. gear box
- ▶ Driven by the bull gear
- ▶ Specially designed to excite the field of the Main Gen./Alternator



Excitation Control Panel

- ▶ A steel fabricated housing
- ▶ Mounted on seven plug in type cards




Magnetic Amplifiers

Uses Reactors namely,

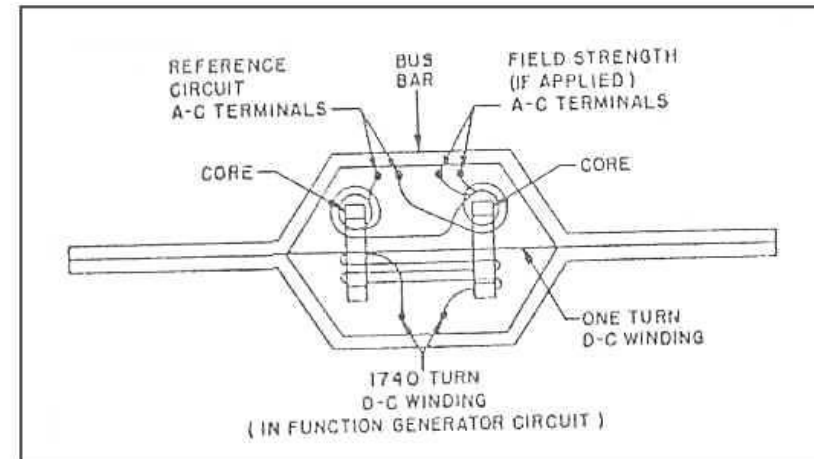1. Armature Current Control Reactor(ACCR)
 2. Voltage Control Reactor(VCR)
 3. Pulse With Modulator (PWM)
- ▶ Magnetic Amplifiers input AC signals comes from Oscillator Card

ARMATURE CURRENT CONTROL REACTOR(ACCR)

- A large bus bar with 02 cores connected in series with the Main Gen.for measuring DC current indirectly.
- Produces ac signal proportional to dc input
- The reactor is calibrated and the complete magnetic structure is sealed in epoxy.




VOLTAGE CONTROL REACTOR(ACCR)

- ▶ Mounted in Excitation panel
- ▶ Produces ac signal proportional to dc input
- ▶ Measures voltage indirectly
- ▶ The reactor is calibrated and the complete magnetic structure is sealed in epoxy



PULSE WIDTH MODULATOR (PWM)

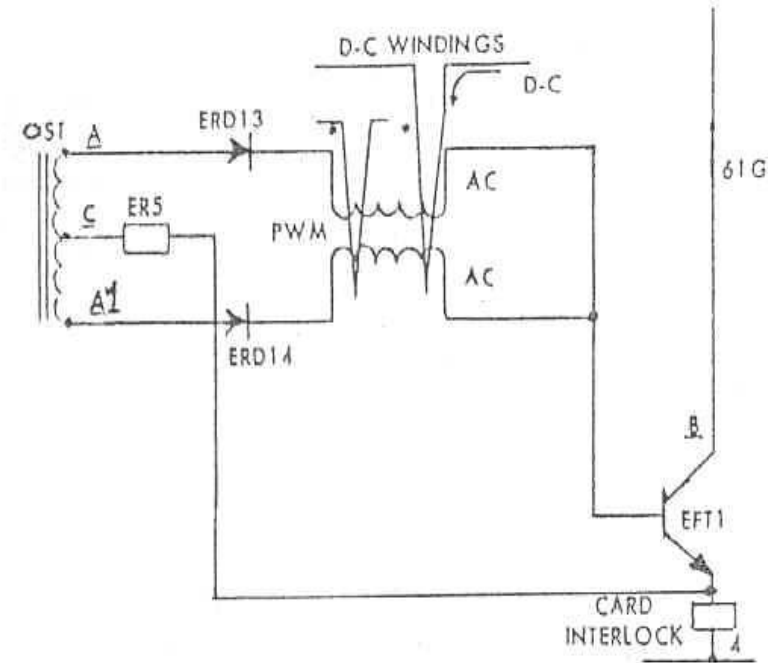
- ▶ A small self-saturating reactor with five dc. control windings and two ac. windings
- Mounted in excitation panel & fed by oscillator
- Control On/Off period of power transistor in switching mode







PULSE WIDTH MODULATOR (PWM)

Five d.c. Windings for feedback control -

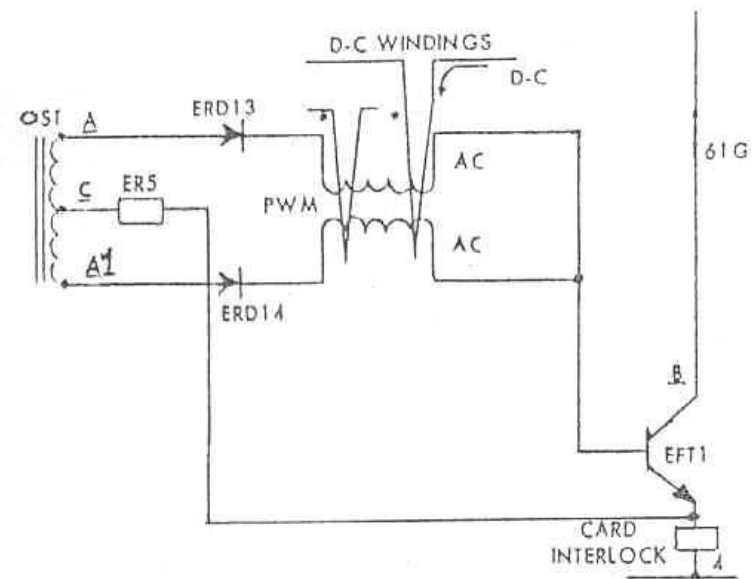1. Exciter suicide and stabilization winding
2. Main excitation control winding
3. Wheel slip power reduction winding
4. Dynamic braking stabilization
5. Dynamic braking anti-negative control




PULSE WIDTH MODULATOR (PWM)

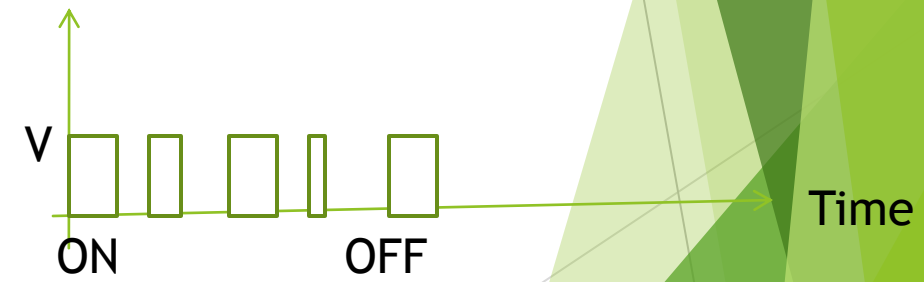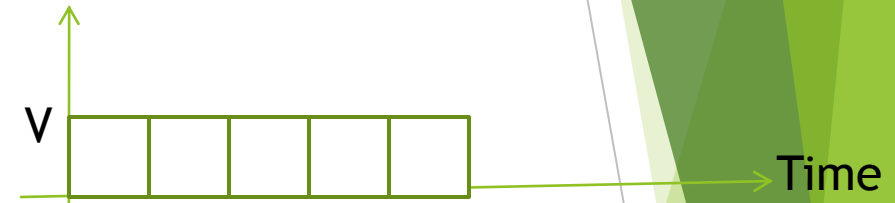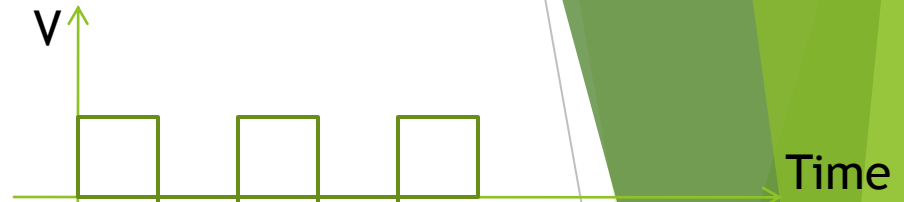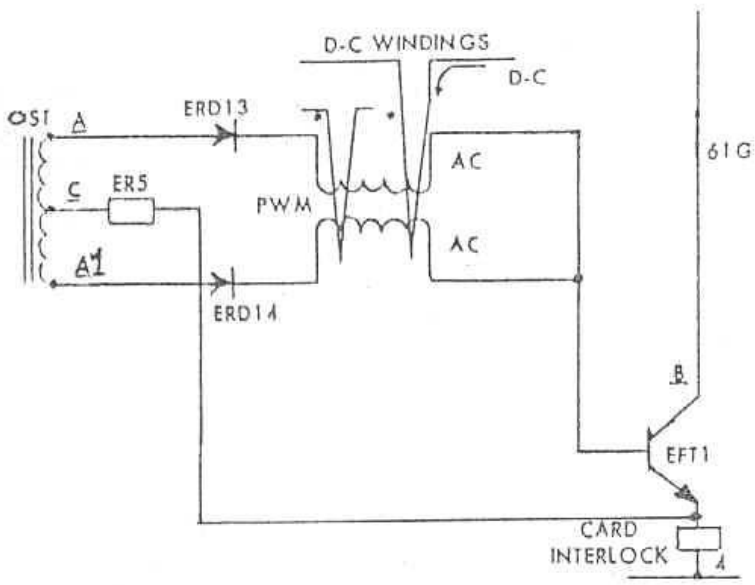


BASIC E-TYPE EXCITATION SYSTEM

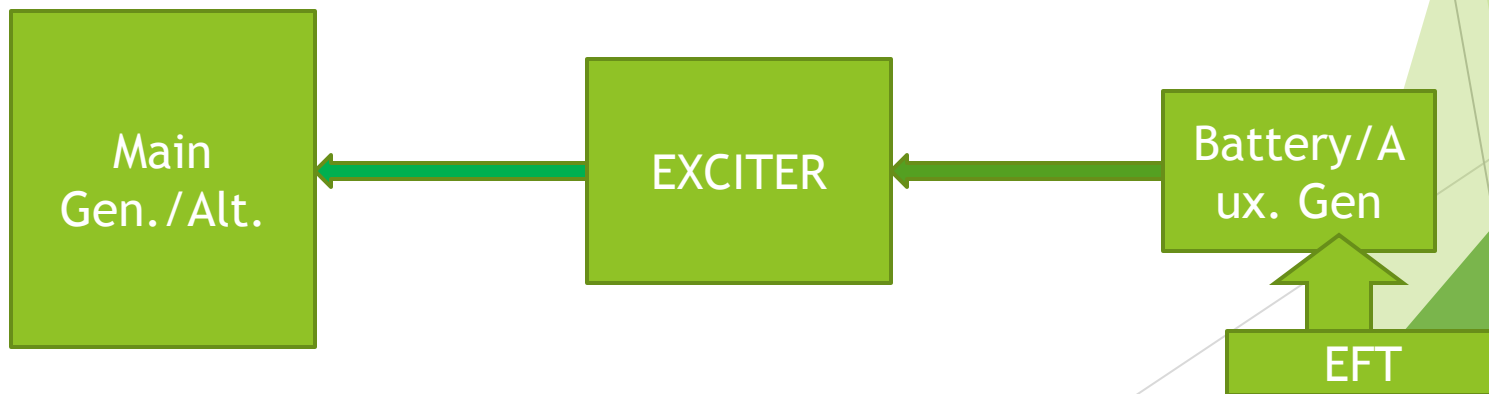- ▶ Main Gen./Alt. excited by Exciter Gen. Current
- ▶ Exciter Gen. excited by Battery/Aux. Gen Current
- ▶ Batt./Aux. Gen. current controlled by a power transistor(EFT) in switching mode



BASIC E-TYPE EXCITATION SYSTEM

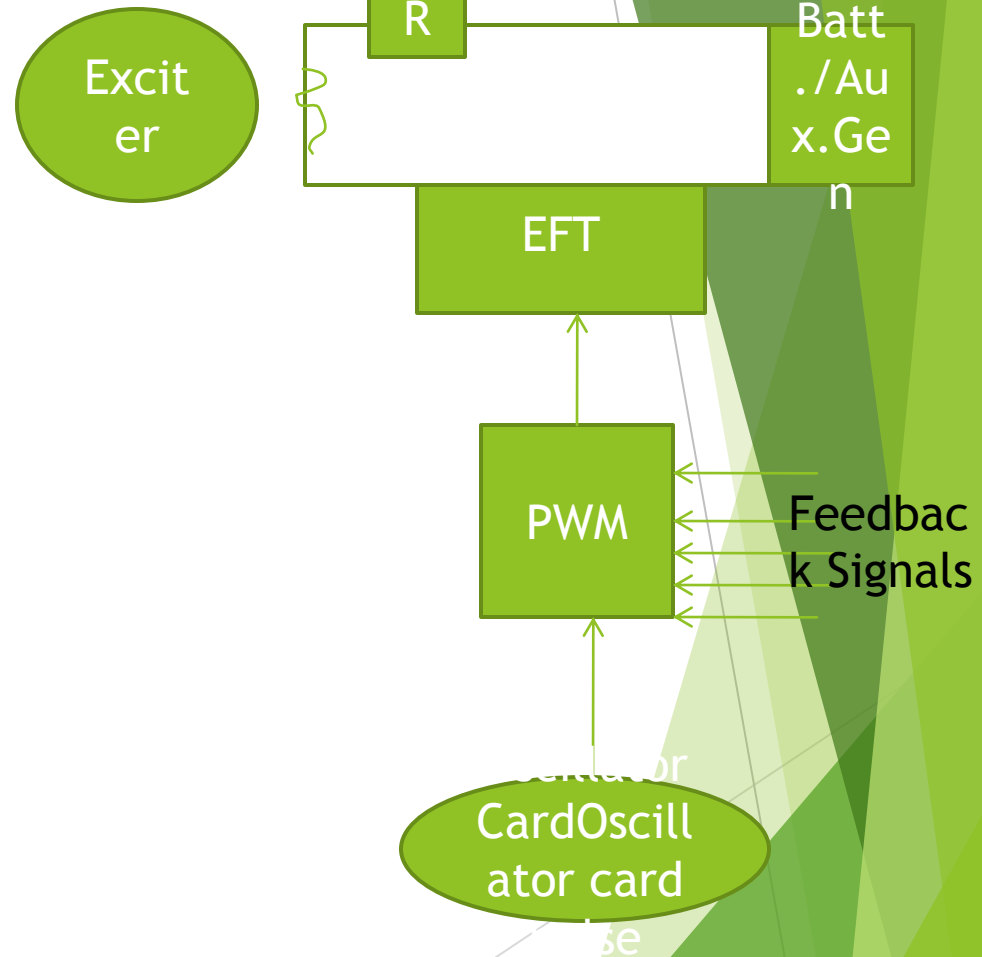
- Power Transistor gets pulses from Oscillator Card and gets 800 times turns ON & OFF in 1 sec.
- ON & OFF period is controlled by different feedback dc signals on PWM card
- OFF-period reduces excitation of Main Gen.



CREATION OF VOLTAGE & CURRENT LIMITS


- ▶ Greater of the signals proportional to M/Gen current and M/Gen Voltage are compared with the speed ref. signal in the Mixer Card.
- ▶ Speed ref. signal preset as voltage /Current limit at the given speed
- If the strength of voltage/current signal exceeds a signal will go to PWM .
- Main Gen. Voltage /current reduce and reaches under limits.

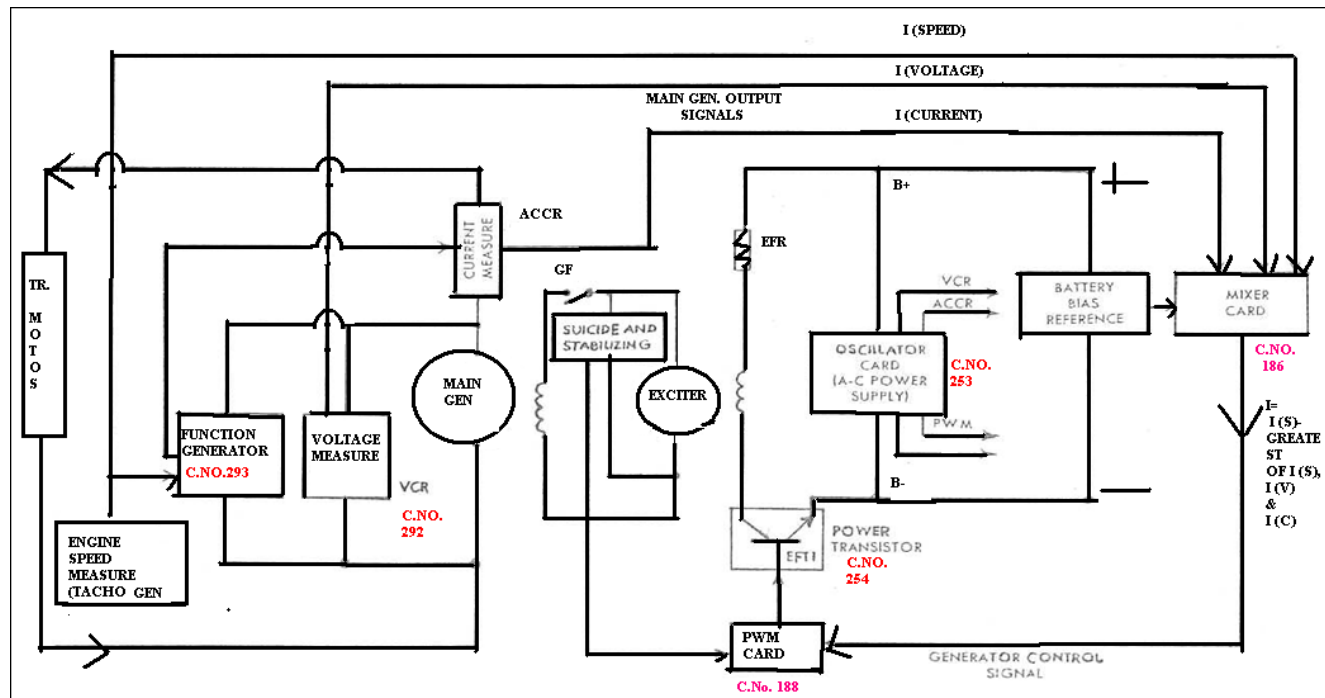BASIC E-TYPE EXCITATION SYSTEM -BLOCK DIAGRAMME




BASIC E-TYPE EXCITATION SYSTEM

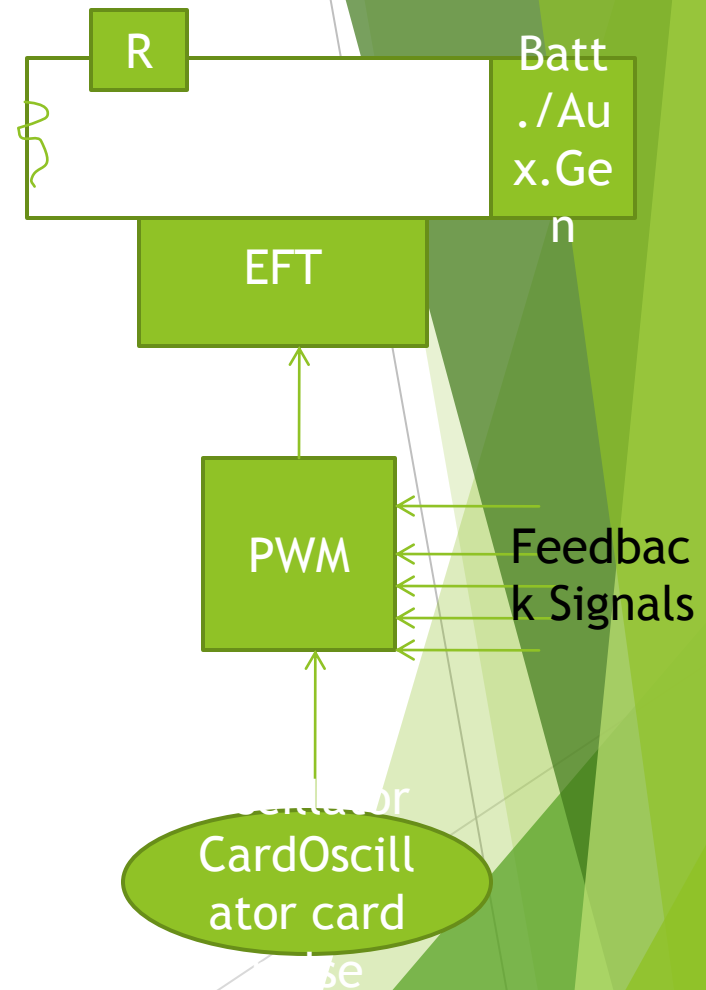- Power Transistor gets pulses from Oscillator Card and gets 800 times turns ON & OFF in 1 sec.
- ON & OFF period is controlled by different feedback dc signals on PWM card
- OFF-period reduces excitation of Main Gen.



CREATION OF APPROX. CONSTANT POWER TRANSMISSION(AT 8TH NOTCH)

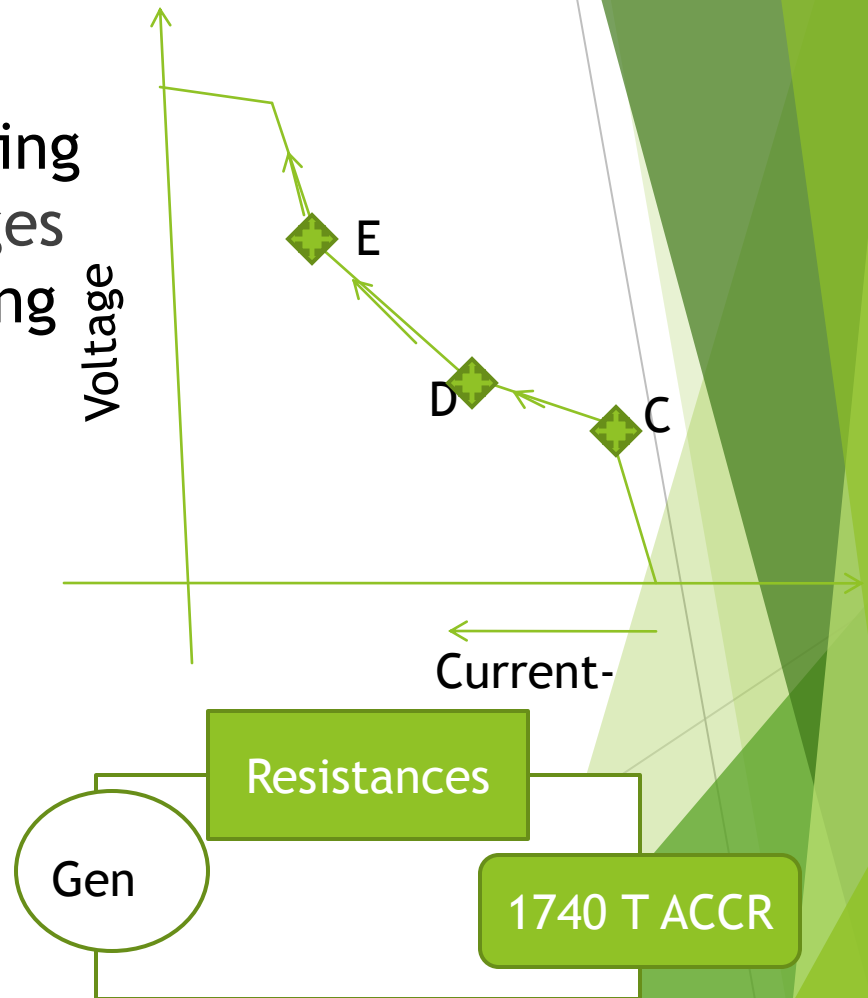
- ▶ Function Gen. allows 3 different current in descending order at different Gen.voltages through 1740 Turn DC winding of ACCR.
- ▶ ACCR gives signals to Mixer card accordingly
- ▶ Current also reduces in descending order.
- ▶ Slope of the Load curve increases



(At C high current at D less current and at D least current passes through 1740 T of

CORNER POINT SUPPRESSION

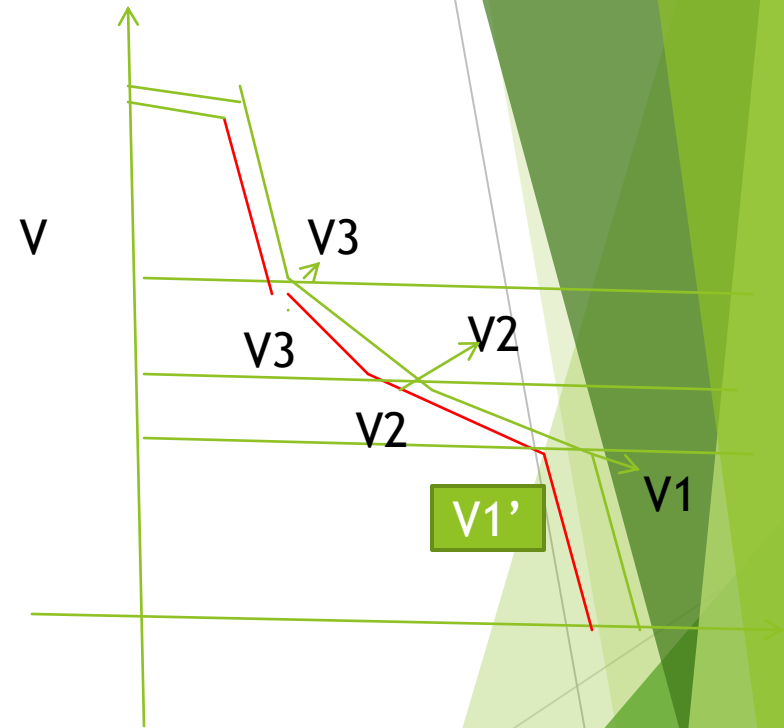- ▶ At lower notches also , slope changes at $V1, V2$ & $V3$ voltages
- ▶ Creates crowding of curves.
- ▶ Suppression circuit inside Function Gen. operates
- ▶ Changes the slope at less voltages $V1', V2'$ and $V3'$ than higher notch voltage
- ▶ Creates separate and better notch curves




OBJECTIVE: Dynamic Brake System

- ▶ Dynamic Brake system :Advantages
- ▶ DC motor into a dc generator
- ▶ Different auxiliary systems associated with Dynamic Brake
- ▶ Distribution of armature and field currents of all six TMs during the application of DB..
- ▶ Explain Braking Torque, efforts and characteristics?
- ▶ Dynamic Brake operation
- ▶ Dynamic Brake Relays and BKCP

DYNAMIC BRAKE - INTRODUCTION

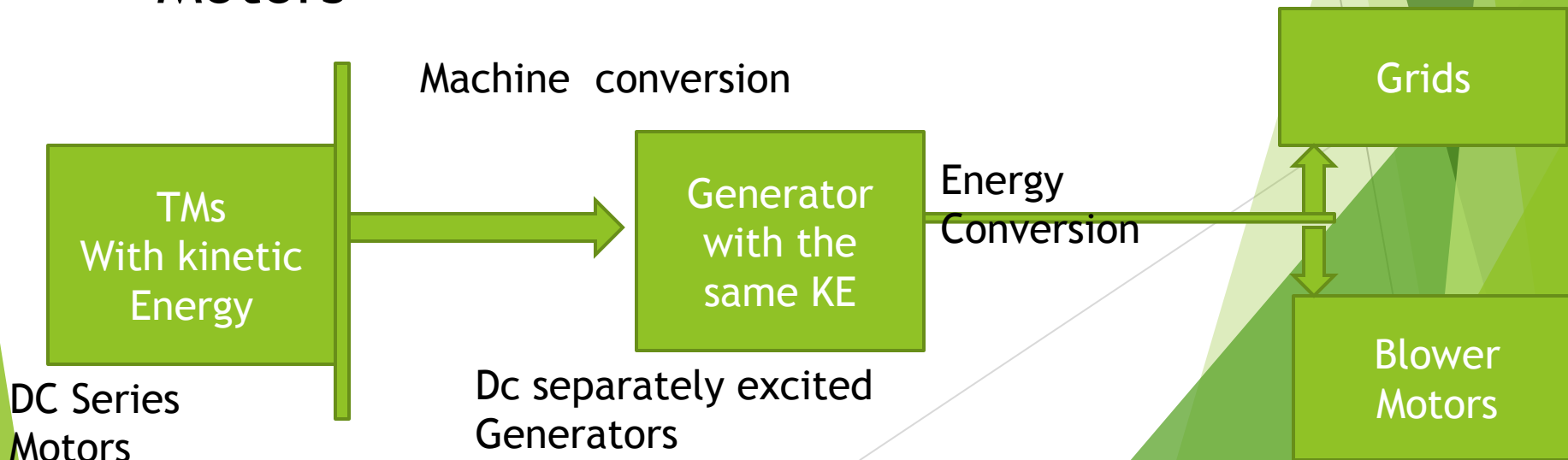- An auxiliary brake
- Not effective at low & high speeds
- ▶ When applied TMs-
 1. Converted into Generators
 2. Gives supply to Grids & Blower Motors



DYNAMIC BRAKE INTRODUCTION

▶ GRIDS & BLOWER MOTOR

Grids




Dynamic
Brake
Blower
Motor

CONVERSION OF TM (DC MOTOR) INTO GEN. (DC GENERATOR)

Conversion is possible because both
have

- Same construction
- Same design
- Same components

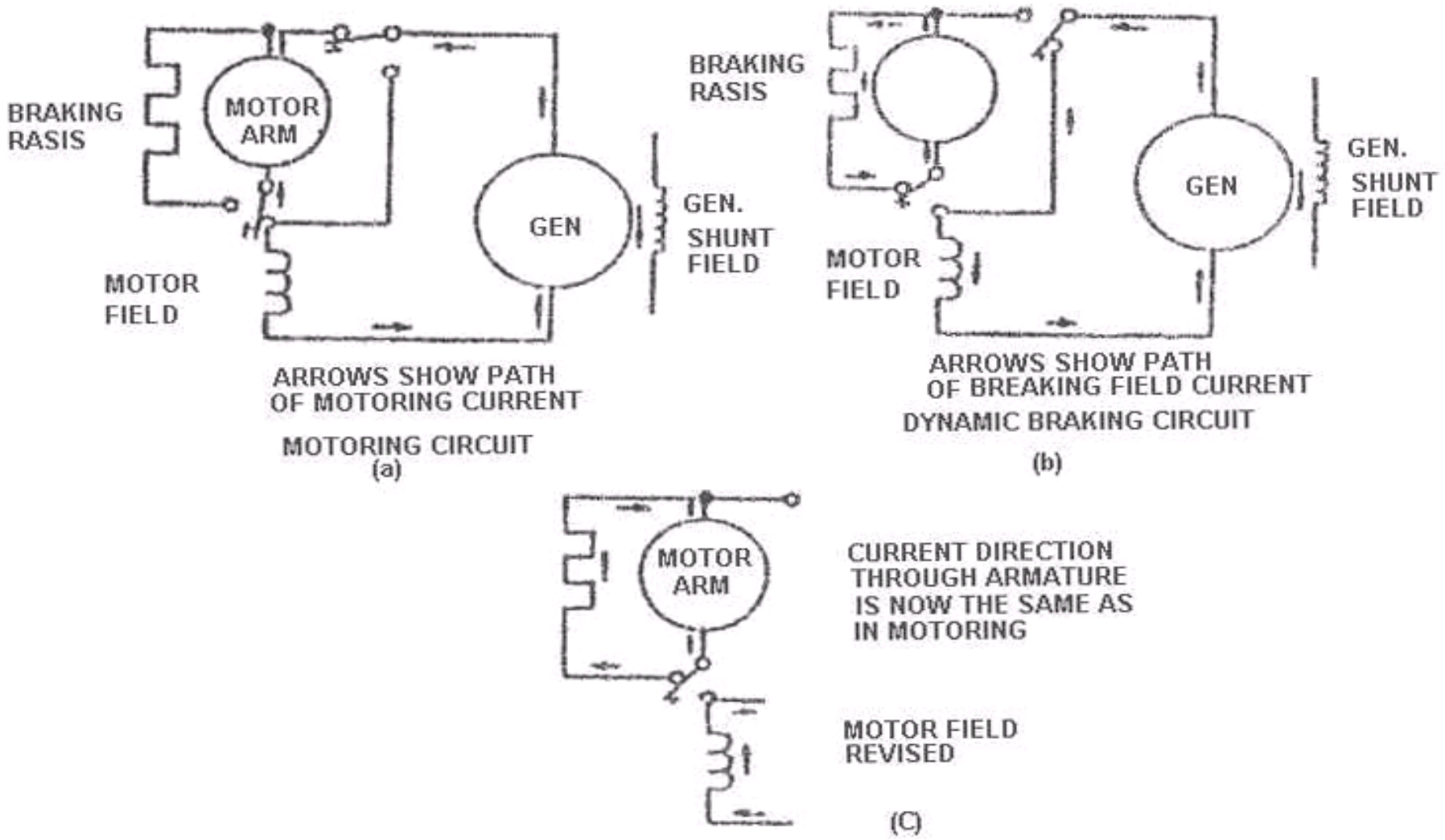CONVERSION OF TM INTO GEN DURING DYNAMIC BRAKE



Conversion of TM into GEN (Showing only for one TM)

BRAKING TORQUE

- ▶ Opposite to rotation of TMs
- ▶ Depends on field current & rotor speed
($T \propto I_{\phi} \omega$)
- ▶ I_{ϕ} — More M/Gen. voltage more field current
- ▶ ω — More loco speed , more rotor speed

BRAKING TORQUE

▶ Direction

- Opposite to rotation of TMs

▶ Dependency

- rotor speed & Field current

▶ Limitation

- Torque increases, Armature voltage & Current also rises to danger mark.

BRAKING TORQUE

UP TO 35/40 KM -


- Speed increases ,
- TM armature voltage/current increases,
- Braking Torque increases

BRAKING TORQUE

BEYOND 35/40 KM-

- ▶ Speed increases
- ▶ Main gen. excitation decreases by VCR of Ex. Control System
- ▶ TM armature voltage/current decreases
- ▶ Braking Torque decreases

BRAKING EFFORT & CHARACTERISTICS

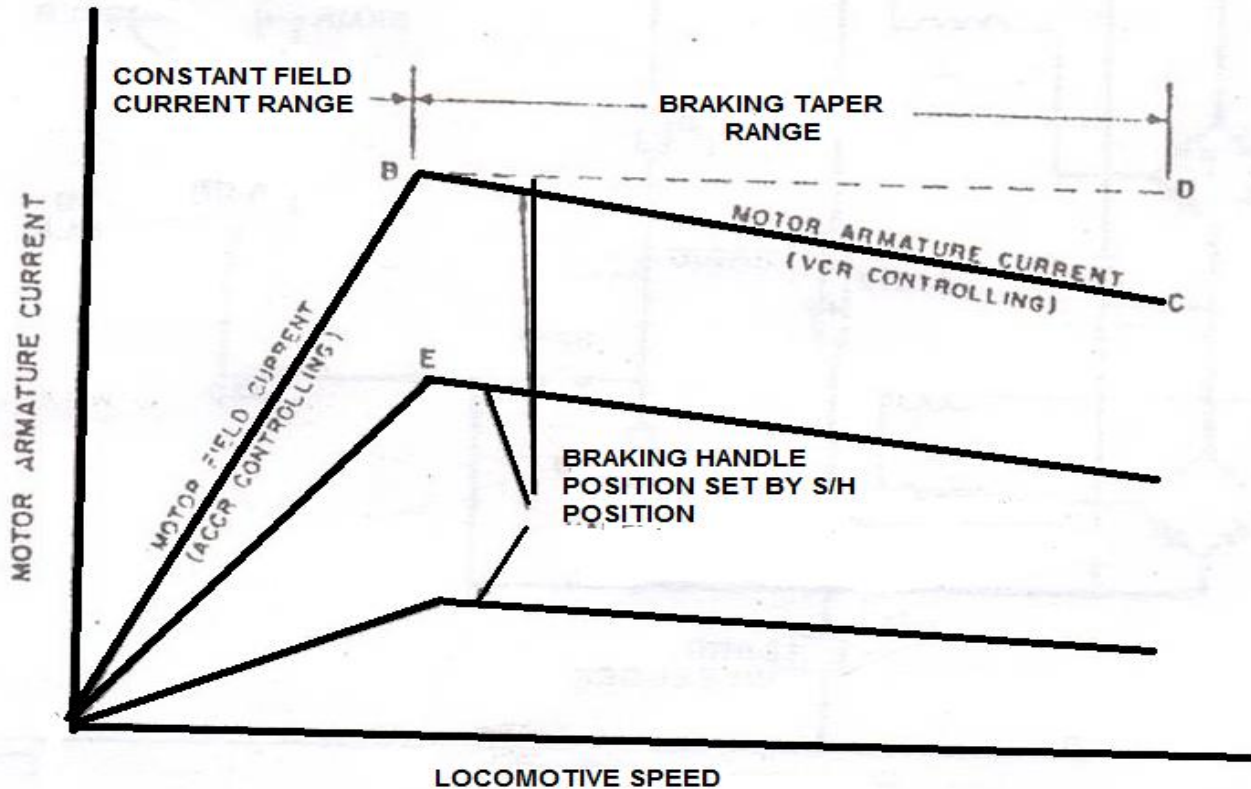

DYNAMIC BRAKING TRACTION MOTOR CHARACTERISTICS

DYNAMIC BRAKE APPLICATION


Causes-

1. BKT switch operation
1. Braking relays (BKR1, BK2 & BKR3) operation
1. BKCP set up.

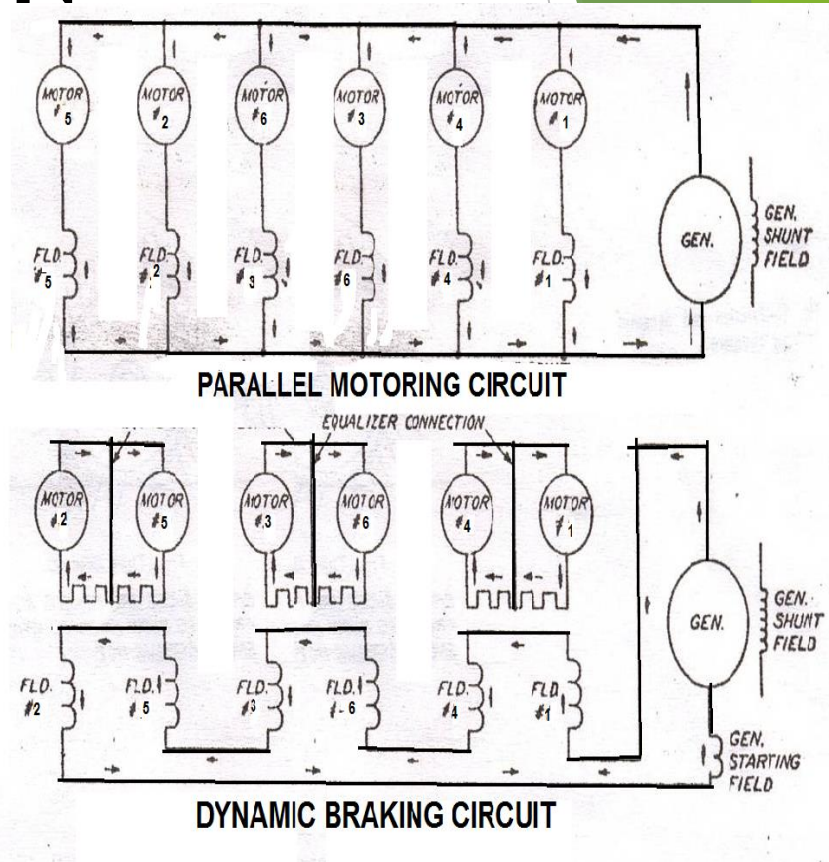1. BKT SWITCH OPERATION

Brings -

- ▶ Fields into series across the M/Gen
- ▶ Armatures into different pairs cut off from Main Gen.
- ▶ Grids & BKBL into Armature Circuit



BKT SWITCH -COMBINATION OF CONTACTORS



LOCATED BELOW POWER CONTACTORS ON FRONT PANEL


2. BRAKING RELAYS OPERATION

Modifies-


- ▶ Engine speed setting
 - 4th notch speed at IDLE
- ▶ Excitation Control System
 - Speed ref. signal to mixer card replaced by braking control signal

CIRCUIT OPERATION-I

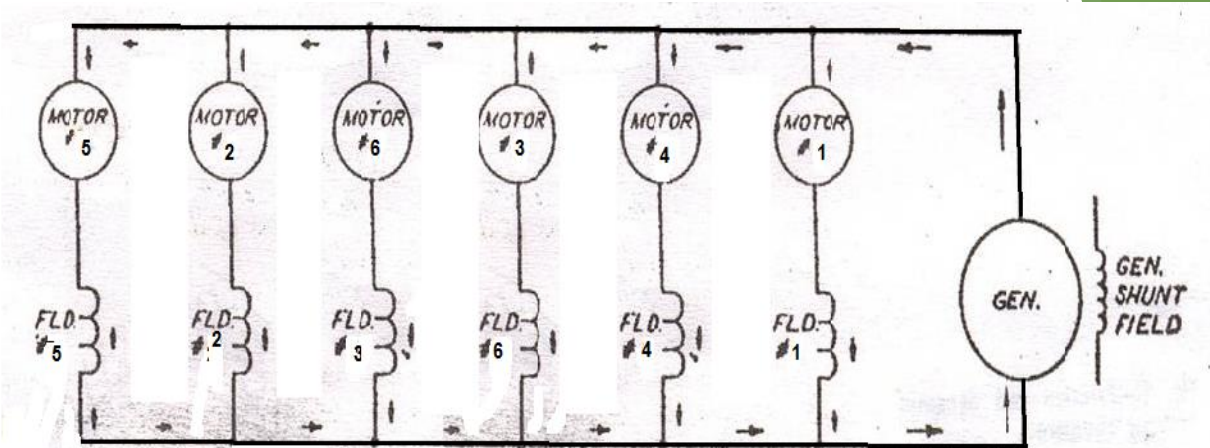Simplified Diagram for Dynamic Brake Operation




PARALLEL MOTORING CIRCUIT

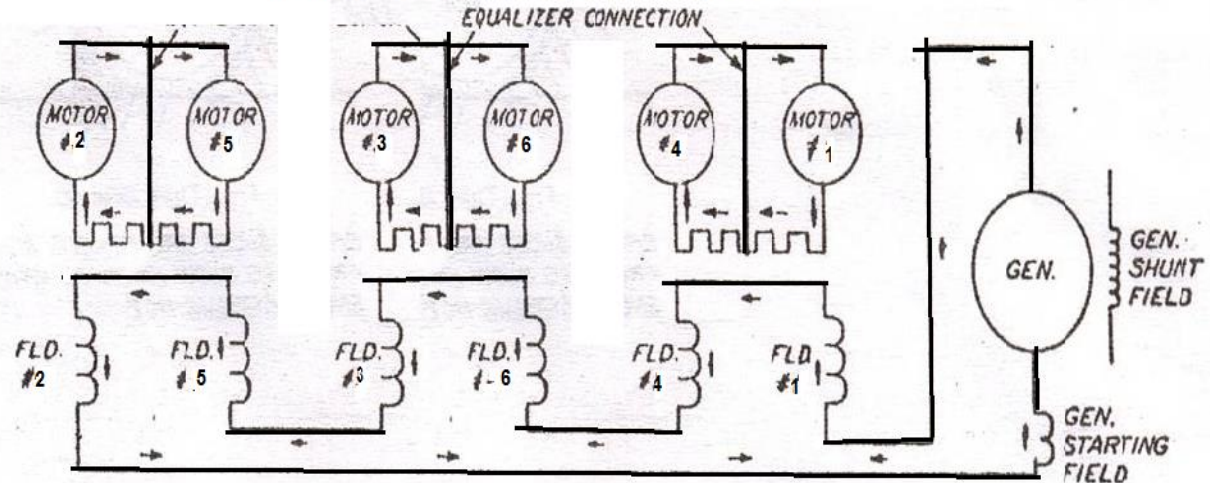


DYNAMIC BRAKING CIRCUIT


CIRCUIT OPERATION-II

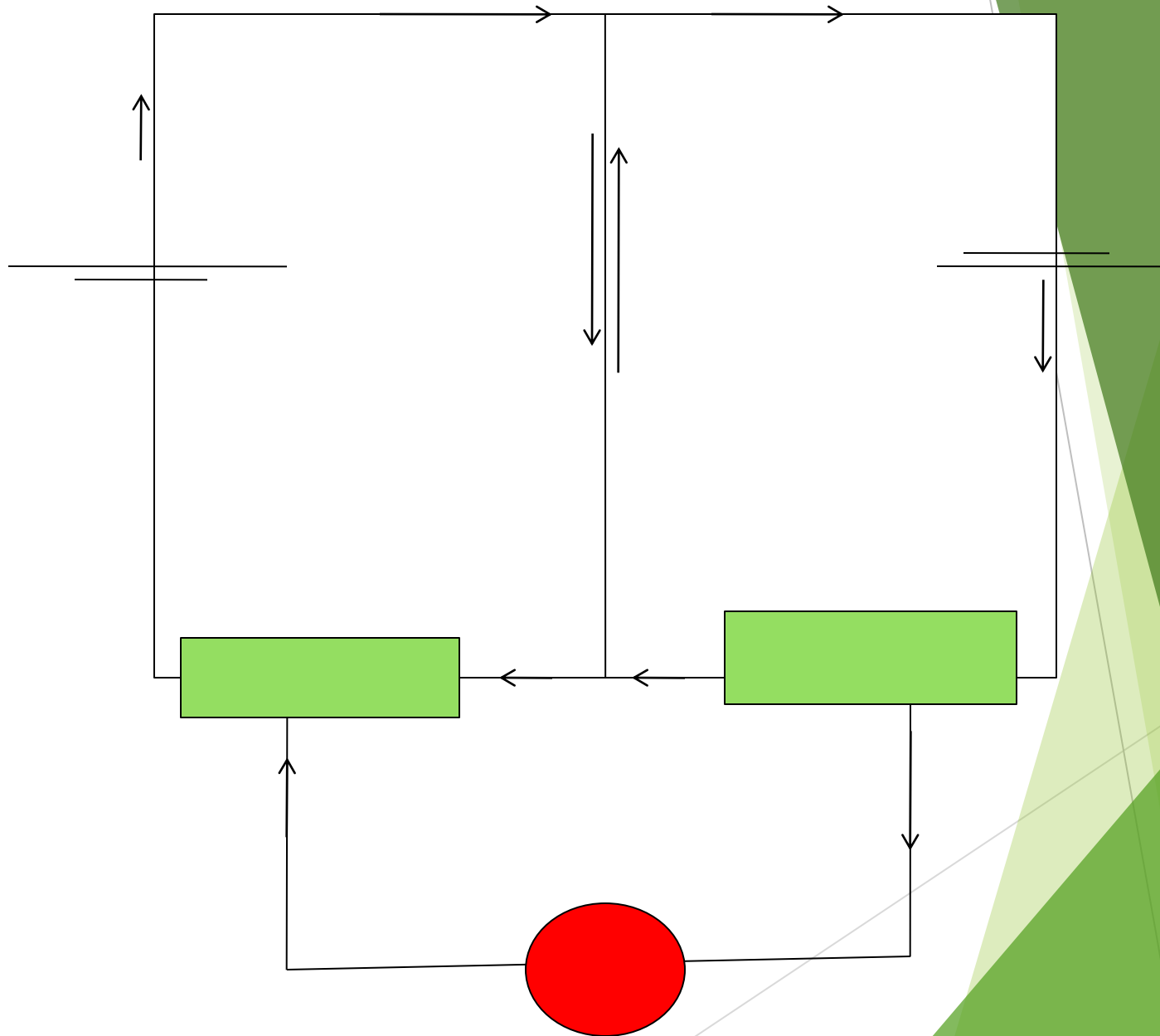


CIRCUIT OPERATION-III

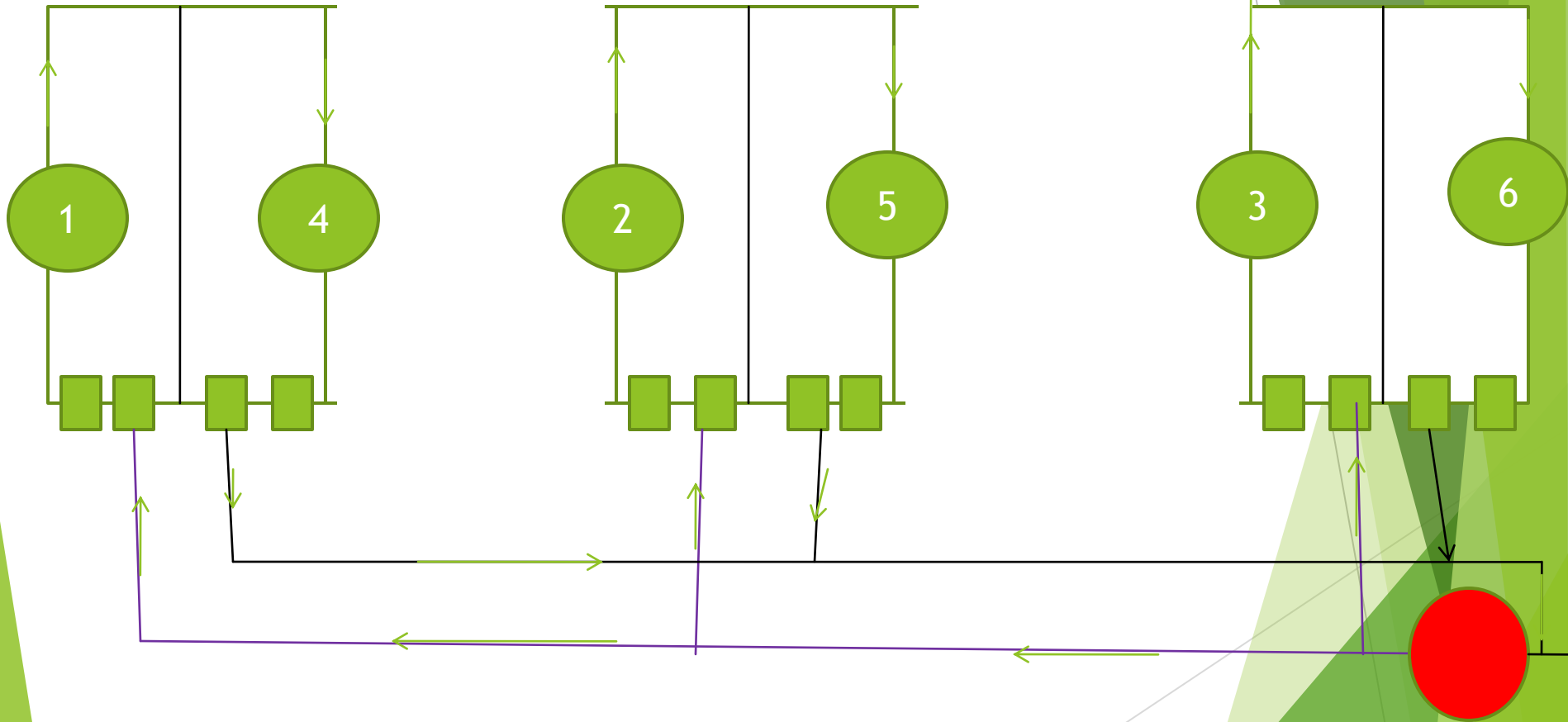

Power Circuit

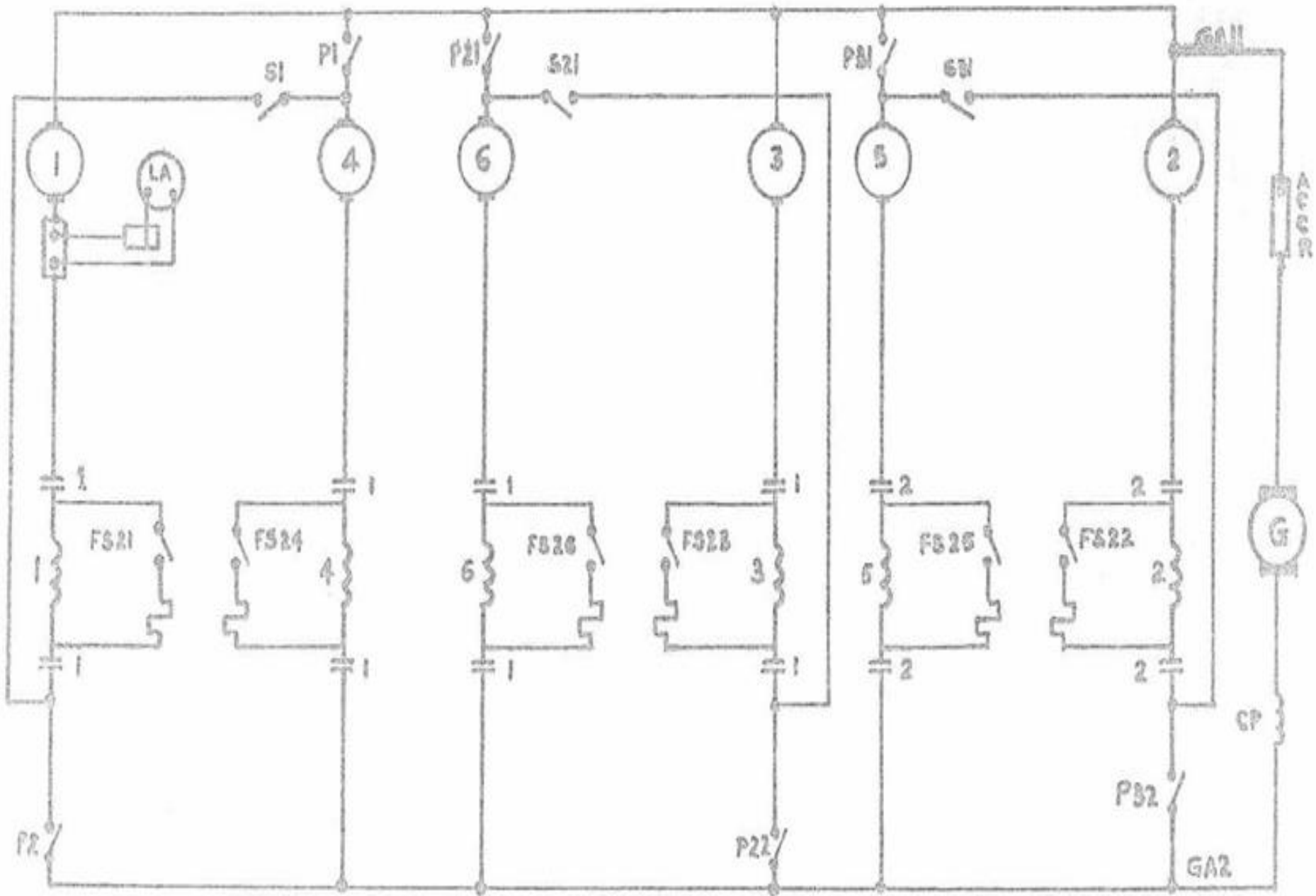

Actual Circuit

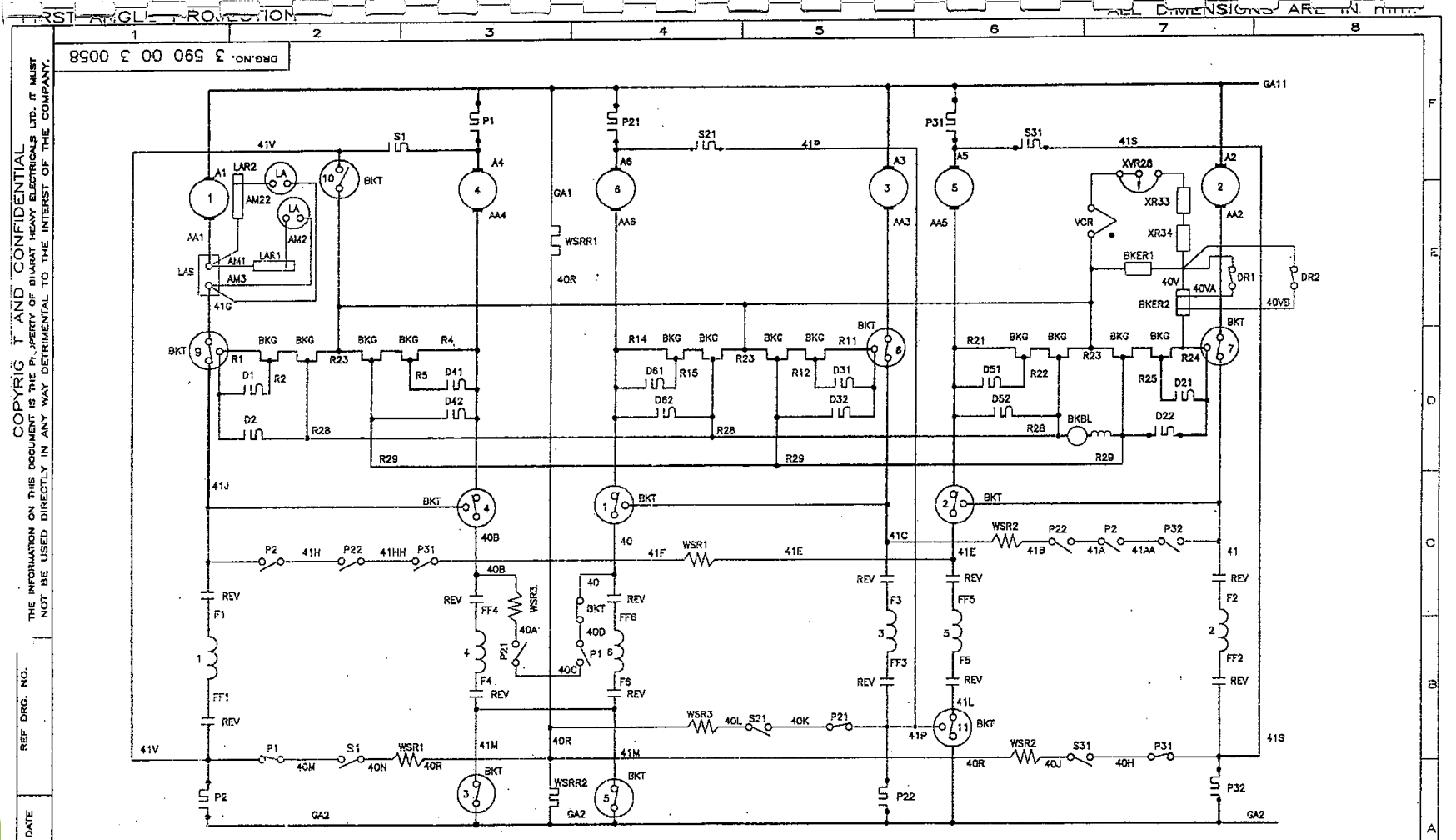

REF. DRG. NO. _____
 SIGN. & DATE _____
 INVENTORY NO. _____
 COPYRIG T AND CONFIDENTIAL THE INFORMATION ON THIS DOCUMENT IS THE PROPERTY OF BHARAT HEAVY ELECTRICALS LTD. IT MUST NOT BE USED DIRECTLY IN ANY WAY DETRIMENTAL TO THE INTEREST OF THE COMPANY.

COMPUTER DRG FILE :- DE58-02
 3100/2750HP, 1100V, BG. DE. LOCOS TYPE WDG 2 AC/DC SYSTEM WITH EXTENDED RANGE OF DYNAMIC BRAKING WITH WOODWARD GOVERNOR

REV	DATE	ALTERED	REV	DATE	ALTERED	DRAWN	NAME	SIGN.	DATE		BHARAT HEAVY ELECTRICALS LIMITED		CARD CODE		
		CHECKED			CHECKED						BHOPAL		REV. NO.	00	
		APPROVED			APPROVED	CHECKED	S.K. RAJ		7-9-99		TITLE		NO. OF SHEETS	38	
DISTRIBUTION OF PRINTS							APPROVED	N.H. JAIN		7-9-99	MAIN POWER MOTOR		SHEET NO.	02	
OFFICE COPY							1				DEPT.	CODE	M.O.NO.	DRG. NO.	3 590 00 3 0058

3.BRAKING CONTROL POTENTIOMETER (BKCP) SETUP

BKCP-

- A variable rotatory resistance
- Fitted in the bottom of the control stand
- Rotate with SH movement
- Controls braking control signal
- Bring down Main Gen. voltage from 1.8 V to 30V

AUXILIARY SYSTEMS

- ▶ Grid Cooling

- By Blower Motor

- ▶ Traction Motor Cooling


- By FTTM & RTTM Blowers , rotate proportional to Engine speed.

DYNAMIC BRAKE - ADVANTAGE

- ▶ Smooth & continuous control
- ▶ Minimum wears on brake block & Wheels

DYNAMIC BRAKE OPERATION

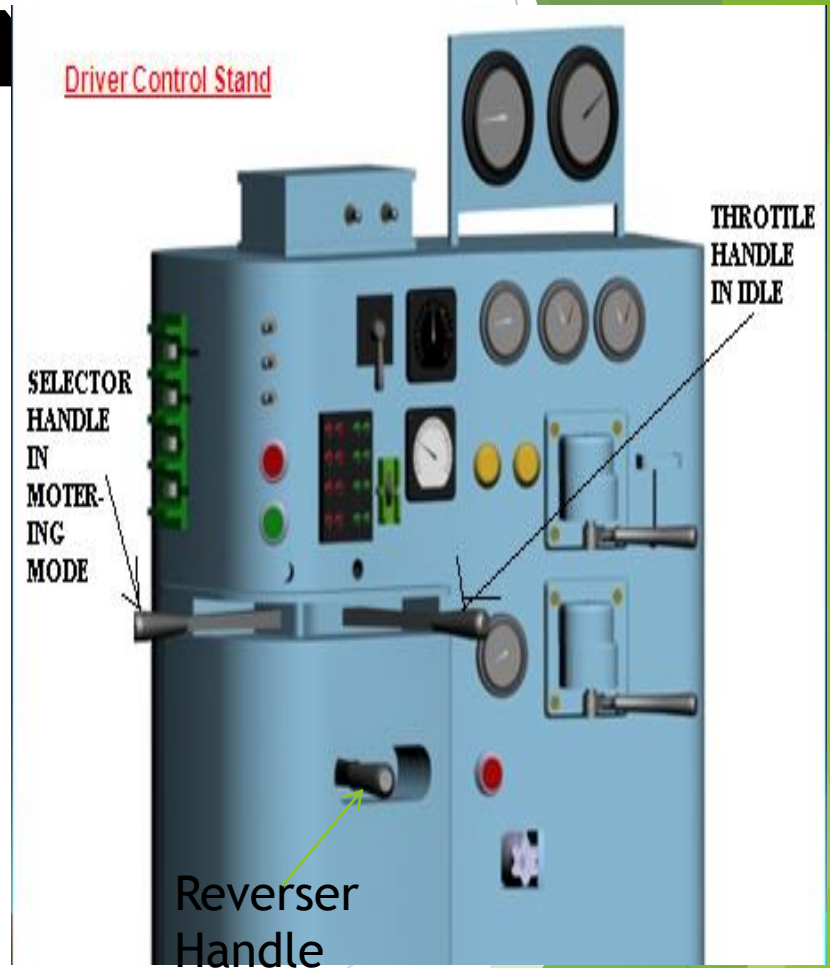- ▶ TH to IDLE
- ▶ RH to forward or backward
- ▶ SH to Dyn. Braking mode
(from 'off' to Big 'D' to Small 'D')



TRAIN BRAKING WITH DYNAMIC BRAKE

- ▶ Dynamic brake circuit include Dynamic brake interlock magnet valve(BKIV)
- ▶ BKIV is a part of loco air brake
- ▶ When applied dynamic brake the loco air brake will not work

THANKS